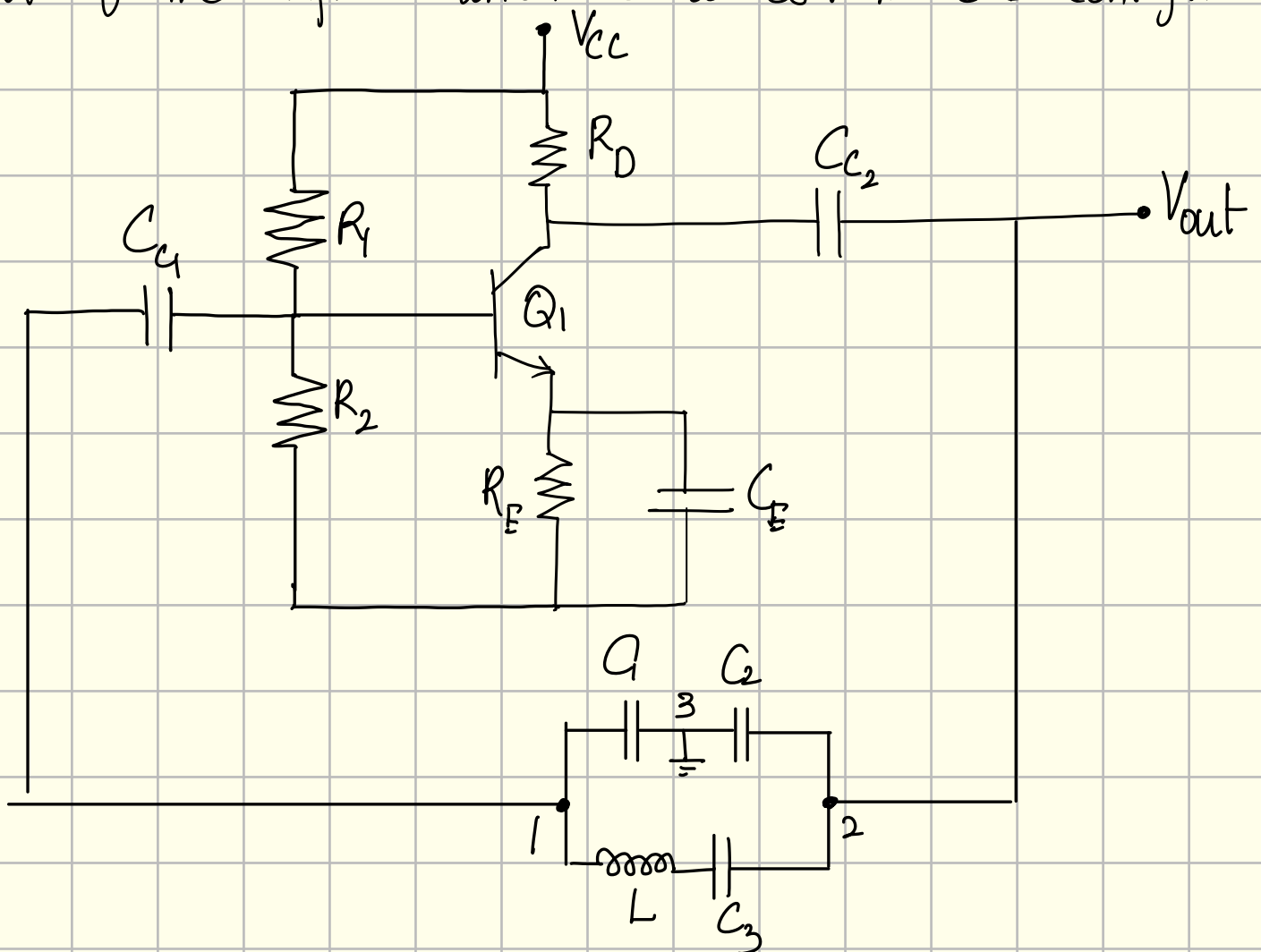


Clapp Oscillator

- much like Colpitt's oscillator with the capacitive voltage divider producing the feedback signal.
- Gives much better stability compared to Colpitt's oscillator.
- The capacitors C_1 and C_2 provide the feedback to input of the amplifier which is a BJT in C-E configuration.



- So in the feedback network, the potential at 2 gets inverted when it reaches point 1 due to the fact it's grounded at point 3. This introduces a 180° phase shift which gets added to the 180° phase shift of the inverting amplifier to produce a total

phase shift of 360° .

• Total $C = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}}$, the C_3 used is a very


small value so that $\frac{1}{C_3} \gg \frac{1}{C_1}$ and $\frac{1}{C_2}$ which get

affected by the parasitic capacitances of the BJT so adding C_3 provides stability to the circuit

$$f = \frac{1}{2\pi \sqrt{LC_3}}$$

• In high frequency oscillators, a HF choke is used in place of R_c which provides a high impedance without dissipating power which provides good output voltage swing. It reduces static power loss and improves Q factor of the oscillator for a purer sine wave.

Equivalent circuit of LC Oscillator

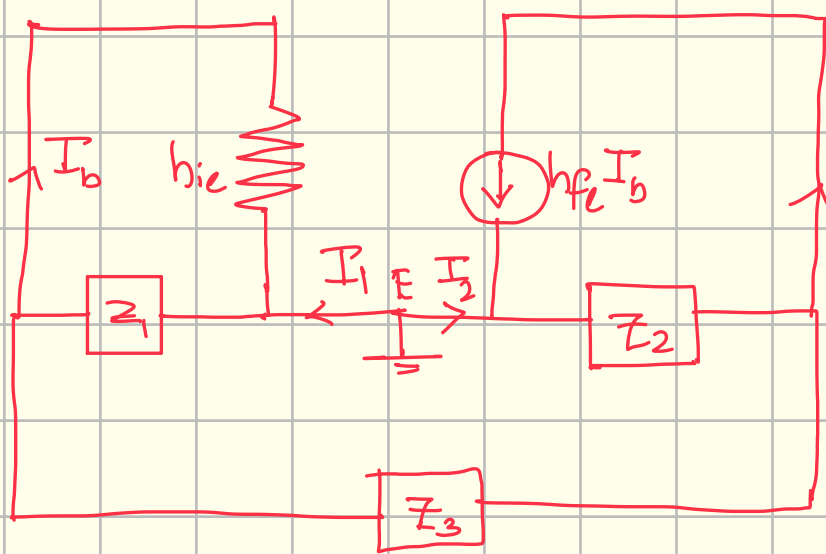

$Z' \rightarrow$ parallel combination of h_{ie} and Z_1

$$Z' = \frac{Z_1 h_{ie}}{Z_1 + h_{ie}}$$

- Now $Z_L \rightarrow$ the load impedance. This is obtained by Z' in series with Z_3 which is parallel to Z_2 .

$$Z_L = \frac{(Z' + Z_3) Z_2}{Z' + Z_3 + Z_2} \quad \text{or} \quad \frac{1}{Z_L} = \frac{1}{Z_2} + \frac{1}{Z' + Z_3}$$

$$\frac{1}{Z_L} = \frac{1}{Z_2} + \frac{1}{\frac{Z_1 h_{ie}}{Z_1 + h_{ie}} + Z_3}$$

$$Z_L = \frac{1}{Z_2} + \frac{1}{\frac{Z_1 h_{ie} + Z_3 (Z_1 + h_{ie})}{Z_1 + h_{ie}}} = \frac{1}{Z_2} + \frac{Z_1 + h_{ie}}{Z_1 h_{ie} + Z_3 Z_1 + Z_3 h_{ie}}$$

Voltage gain without feedback: $A_V = \frac{-h_{fe} Z_L}{h_{ie}}$

- For the feedback network, Output voltage across Z_2 and input voltage across Z' .

$$\beta = \frac{Z'}{Z' + Z_3} = \frac{Z_1 h_{ie}}{h_{ie}(Z_1 + Z_3) + Z_1 Z_3}$$

$A_V \beta = 1 \rightarrow$ Barkhausen's criteria

$$\frac{-h_{fe} \times Z_L}{h_{ie}} \times \frac{Z_1 h_{ie}}{h_{ie}(Z_1 + Z_3) + Z_1 Z_3} = 1$$

Simplifying this equation -:

$$h_{ie}(Z_1 + Z_2 + Z_3) + Z_1 Z_2 (1 + h_{fe}) + Z_2 Z_3 = 0$$

↳ Characteristic equation of oscillator

* pretty sweet.

